
 


Програмируеми Логически Прибори

 


Programmable Logic Devices


Basic Structure



AND Matrix

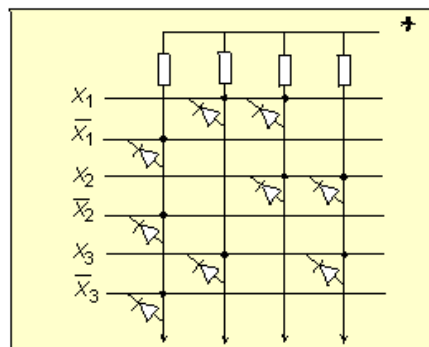


OR Matrix

 


$$Y1 = P1 + P2 + P3 = \bar{X1}\bar{X2}\bar{X3} + X1.X3 + X1.X2$$

$$Y2 = P2 + P4 = X1.X3 + X2.X3$$

 
Implementation Boolean Equations - an Example




PLD Standard Notations

 


Programmable Connections

 


PLA Matrix

 


PLD with Register

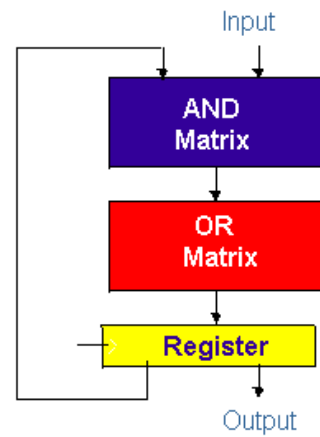


PROM Architecture

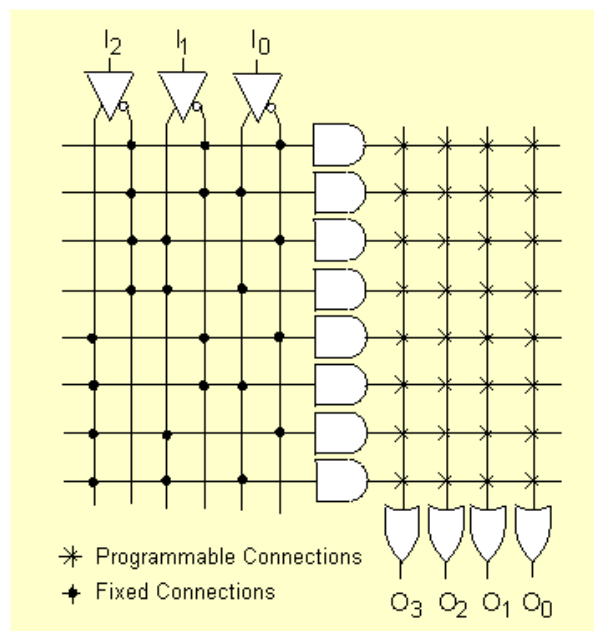


PAL Architecture

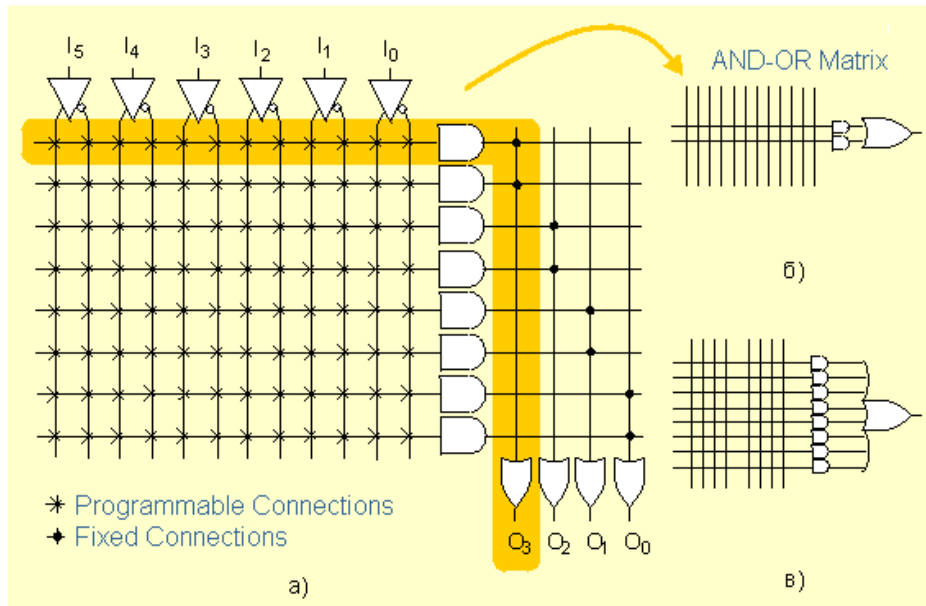


Input/Output Types in PAL

 

Programmable
Input/Output

 


Register Output

 

Output
Programmable
Polarity

Input Output Macrocell

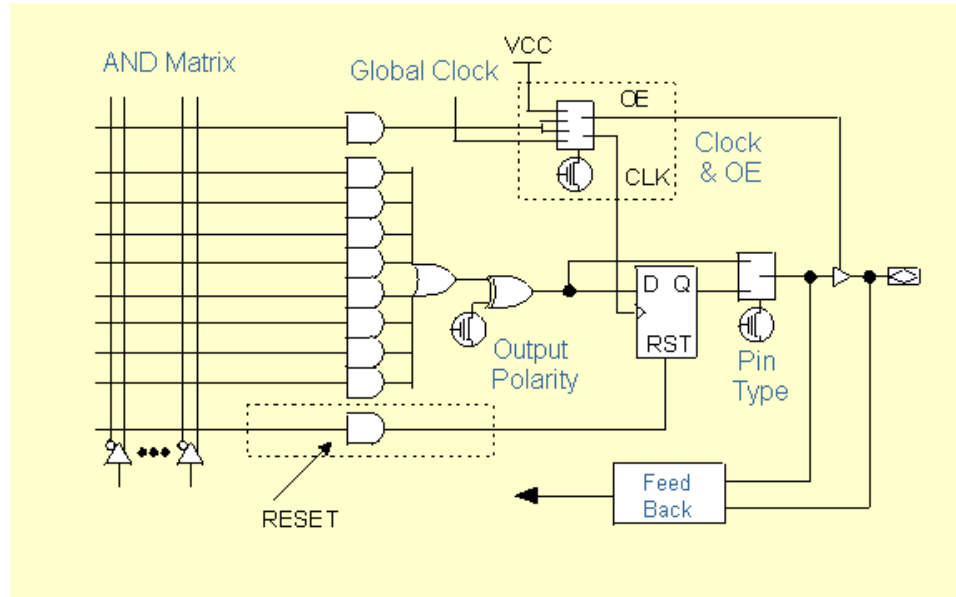

Complex Programmable Logic Devices - CPLD



Economic impact
Concepts and terminology
Design flow in digital VLSI
Field-programmable logic
Appendix I: A brief glossary of logic families

Configuration technologies
Organization of hardware resources
Commercial products
Extensions
Design flow

Complex programmable logic devices (CPLD)

► Overall organization has evolved from purely combinational devices.

a) **PLA**

programmable logic

b) **SPLD**

programmable logic
programmable feedback

c) **CPLD**

configurable I/O cell
programmable interconnect
programmable logic
flip-flops & feedback


equivalent to one SPLD

technological evolution

technological evolution


Figure: General architecture of CPLDs (c) along with precursors (a,b).

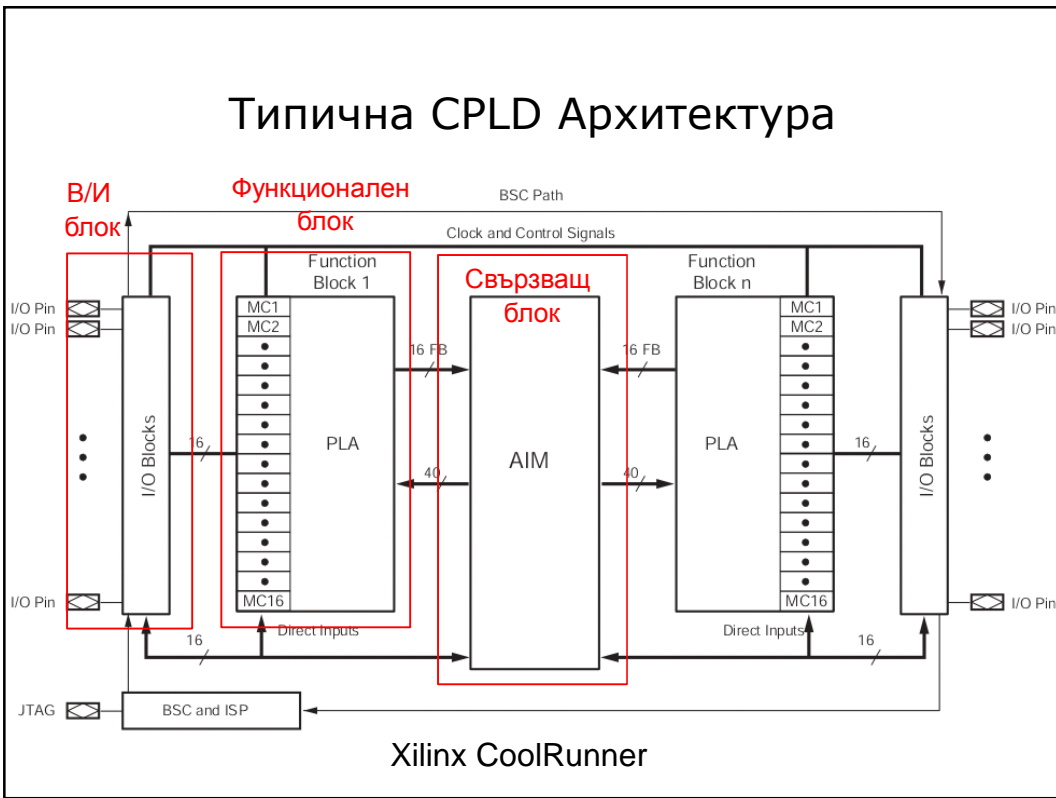© Hubert Kaeslin Microelectronics Design Center ETH Zürich
Introduction to Microelectronics




CoolRunner – Функционален Блок

 
В един CoolRunner чип има от 2 до 32 функционални блока.



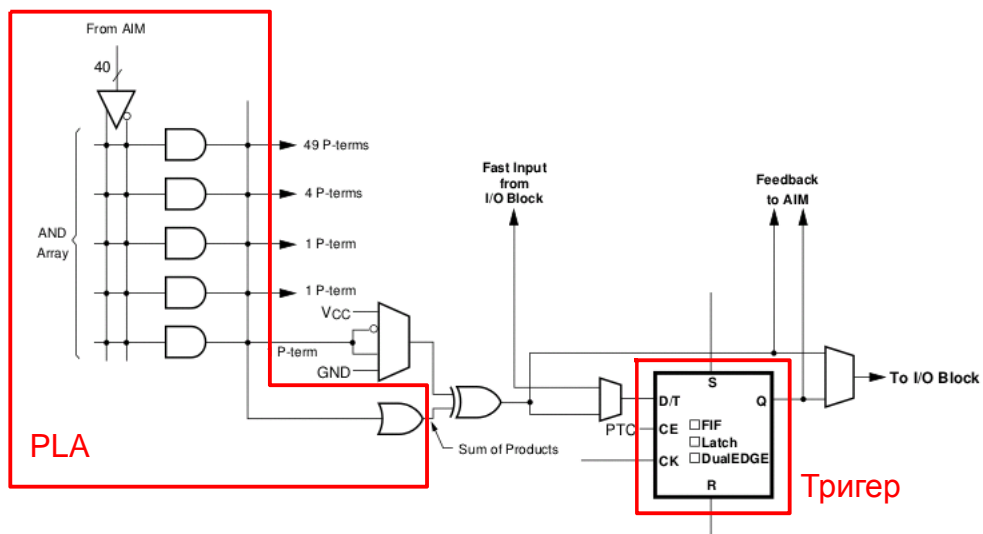
CoolRunner – Макроклетка (опростена схема)



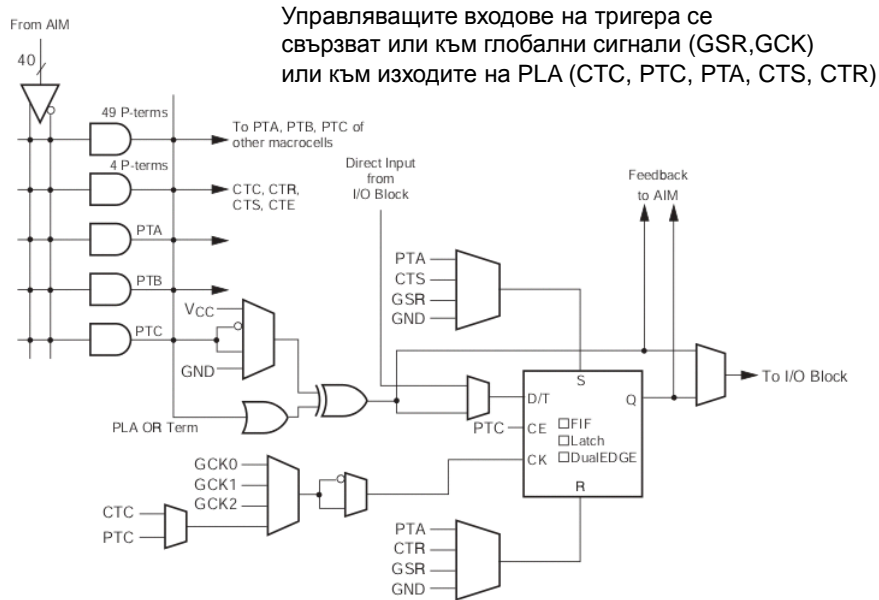CoolRunner - Макроклетка (цялостна схема)




CoolRunner – Входно/Изходен Блок

 

Програмиране на CoolRunner

 Записването на конфигурацията се извършва чрез JTAG интерфейс.



Специални функции на CoolRunner-II

DualEDGE registers

Нарастващ фронт:

```
if(clock'event)and(clock='1')then
```

И по двата фронта:

```
if(clock'event)then
```

Делител

 


Figure 1: CoolRunner-II Clock Divider

```
Component CLK_DIV2 is
  port(
    CLKIN:inSTD_LOGIC;
    CLKDV:outSTD_LOGIC);
end component;

U1:CLK_DIV2
  portmap(
    CLKIN => clk,
    CLKDV => clk_div_by_2);
```

Тригер на Шмит


 


Figure 5: Representation of a Schmitt Trigger Input Buffer

Тригер на Шмит

 

Тригер на Шмит

UCF файл

```
NET <signalname> SCHMITT_TRIGGER;
```

Пример: NET data_in SCHMITT_TRIGGER;

VHDL

```
attribute SCHMITT_TRIGGER:STRING;
```

```
attribute SCHMITT_TRIGGER of <signalname>: signal is "TRUE";
```

Пример:

```
attribute SCHMITT_TRIGGER:STRING;
```

```
attribute SCHMITT_TRIGGER of data_in: signal is "TRUE";
```

В/И Стандарти

Table 9: CoolRunner-II Supported I/O Standards

| | XC2C32 | XC2C64 | XC2C128 | XC2C256 | XC2C384 | XC2C512 |
|--------------------------------------|--------|--------|---------|---------|---------|---------|
| I/O Banks | 1 | 1 | 2 | 2 | 4 | 4 |
| LVTTL | Yes | Yes | Yes | Yes | Yes | Yes |
| LVCMOS33, LVCMOS25, & LVCMOS18 | Yes | Yes | Yes | Yes | Yes | Yes |
| 1.5V I/Os | Yes | Yes | Yes | Yes | Yes | Yes |
| SSTL2-1 & SSTL3-1 | No | No | Yes | Yes | Yes | Yes |
| HSTL-1 | No | No | Yes | Yes | Yes | Yes |

```
NET data_in IOSTANDARD = LVCMOS18;
```

```
attribute IOSTANDARD : STRING;  
attribute IOSTANDARD of data_in : signal is "LVCMOS18";
```

