




# Zener Diode



Semiconductor  
Elements

*Last update 14.04.2020*


# Zener Diode Cases

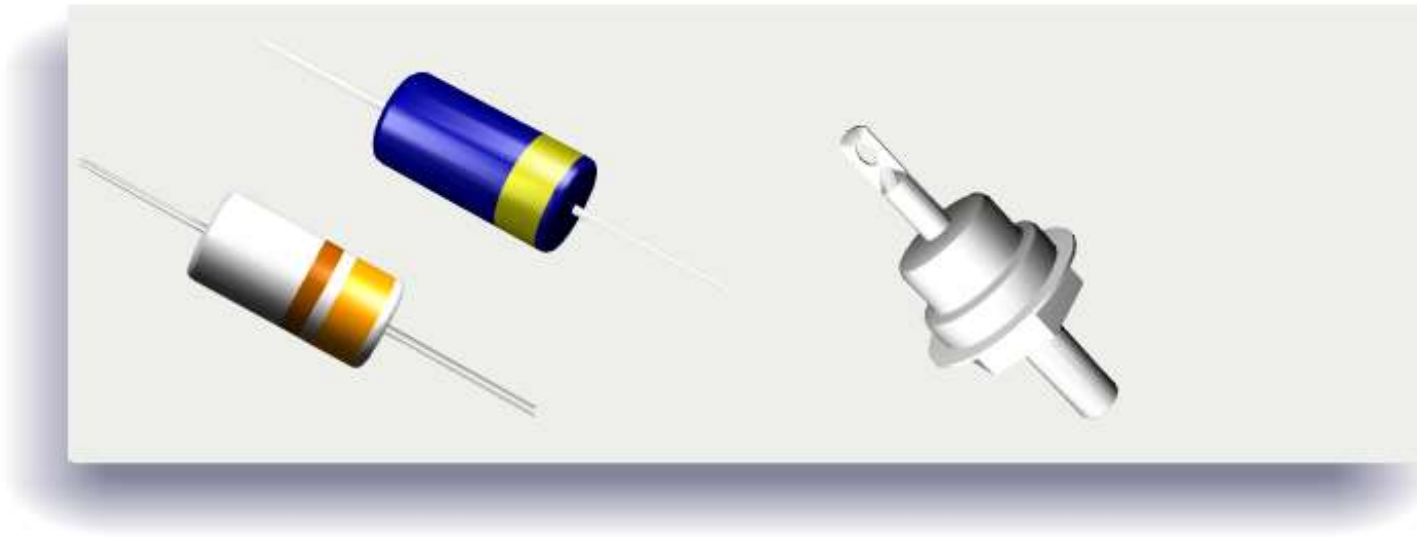

Plastic and glass packages

Metal case for large power


# Basic Zener Diode Feature

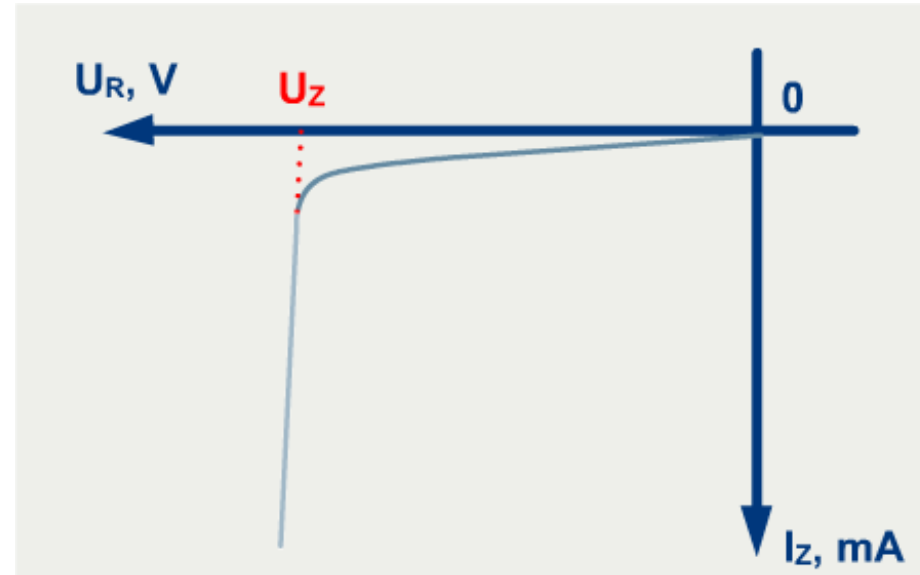

A **Zener diode** is a special-purpose silicon diode optimized for operation in the **breakdown region**.

Once a breakdown occurs the voltage  $U_Z$  across the zener diode becomes almost constant and independent of the current through the diode. By utilizing a constant voltage zener diodes often operate as **voltage regulators**.


# Zener Diode Schematic Symbol

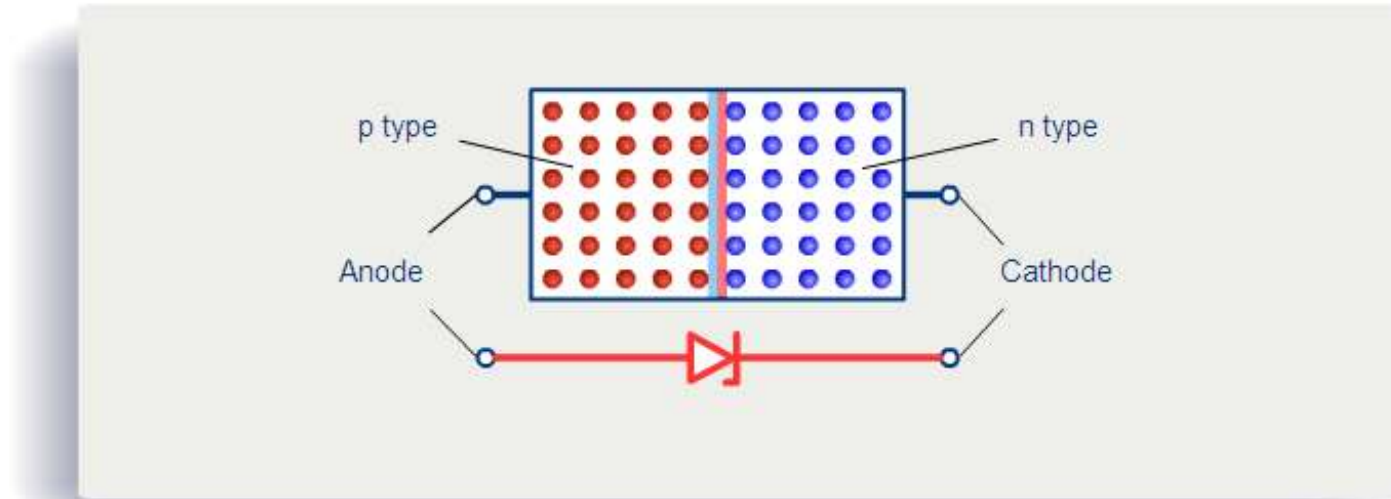

The zener diode has two electrodes. The  $p$ -side is called anode, and the  $n$ -side - cathode.


When zener diode operates in breakdown mode, the cathode must be positive in respect to the anode.

# Zener Diode Mode of Operation

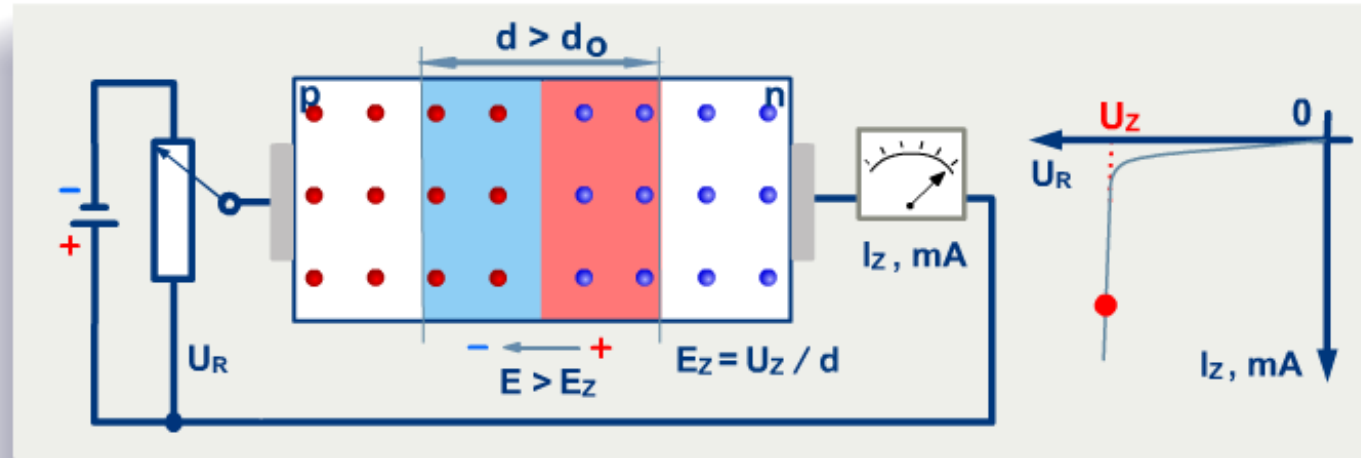


Once the breakdown voltage is reached, a large number of minority carriers suddenly appears in the depletion layer and the diode starts to conduct heavily. This results from two mechanisms known as **avalanche** and **zener breakdown**.

# Avalanche and Zener Breakdown

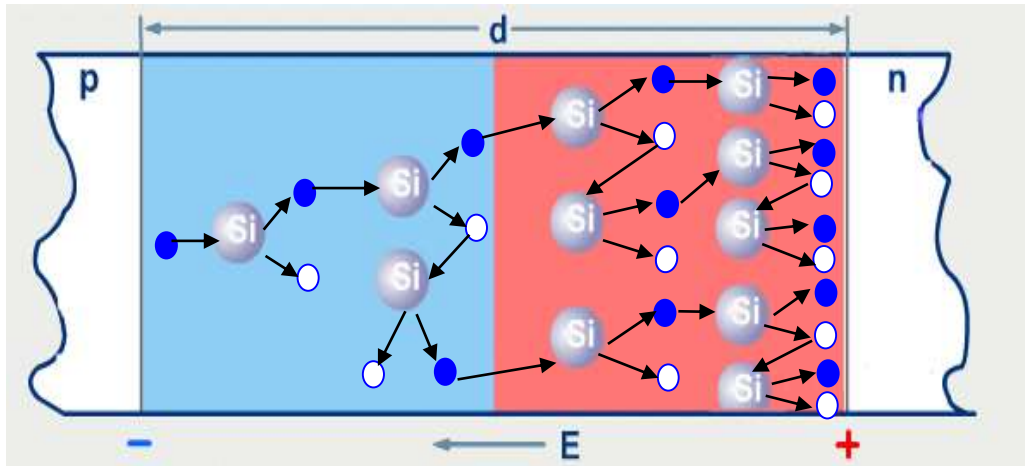


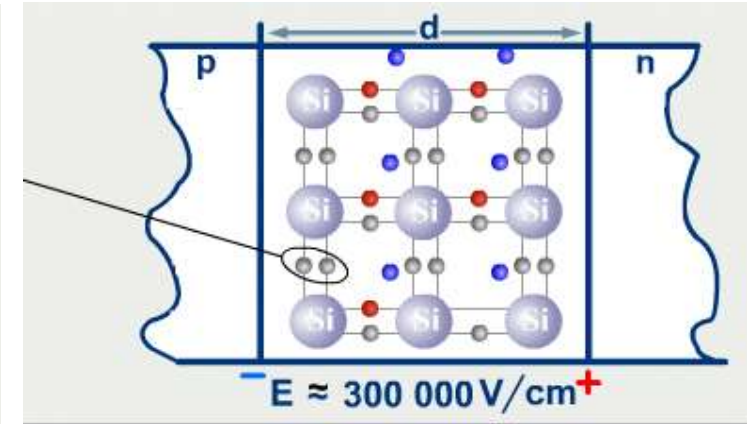Avalanche breakdown occurs in wide depletion layers with a reverse bias **higher than 7V**.



Zener breakdown occurs in very narrow depletion layers with a reverse bias **less than 5V**.


# Zener Diode VA Characteristic

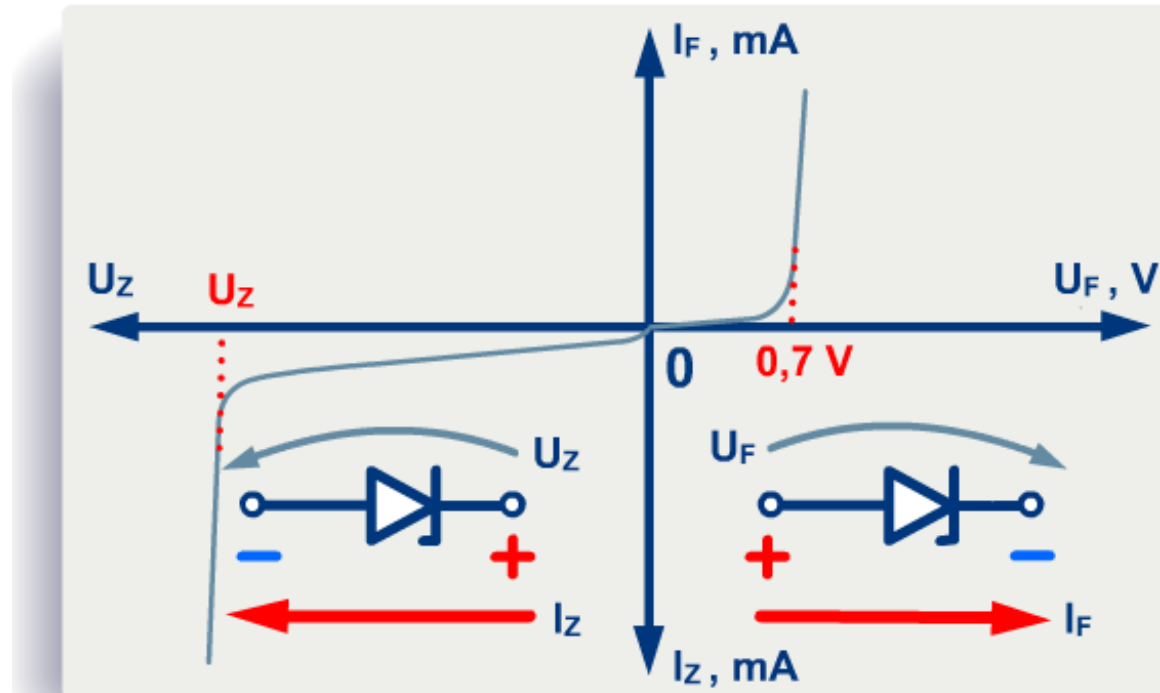

A zener diode can operate in any of the three regions: **forward, reverse and breakdown.**

In the forward region it starts conducting around 0.7 V, just an ordinary Si diode. The reverse current before breakdown is very small. In the breakdown region there is an almost vertical rise in current, where the voltage is almost constant.

# Breakdown Region

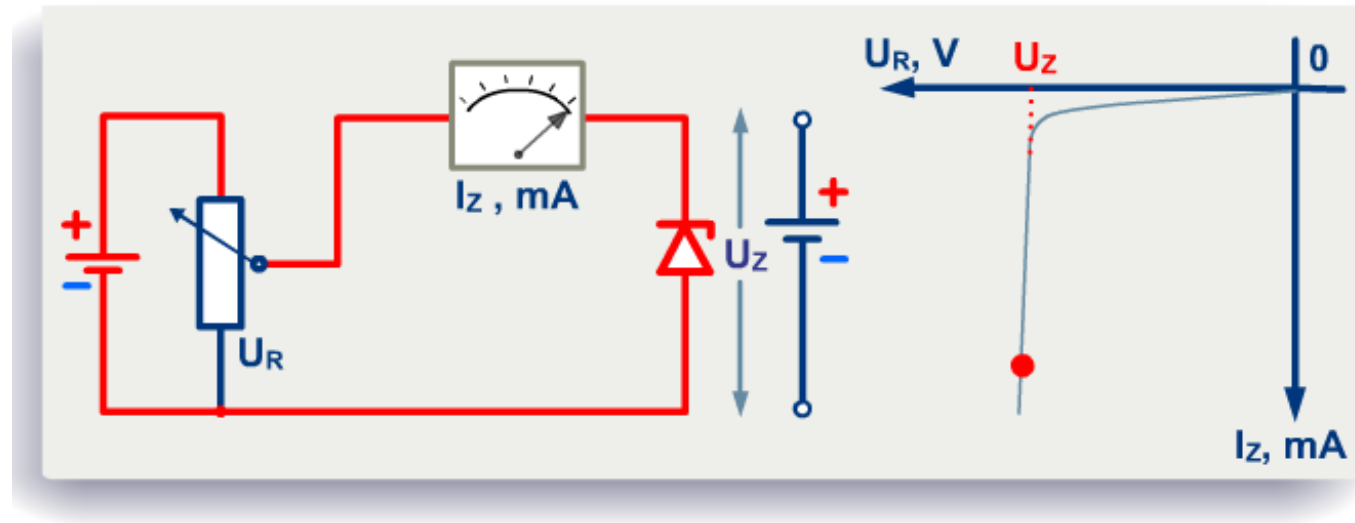


A Zener diode maintains a constant output voltage even though the current changes through it.

In the *breakdown region* a zener diode ideally acts like a battery and can be replaced by a voltage source of  $U_Z$ .




# Load Line

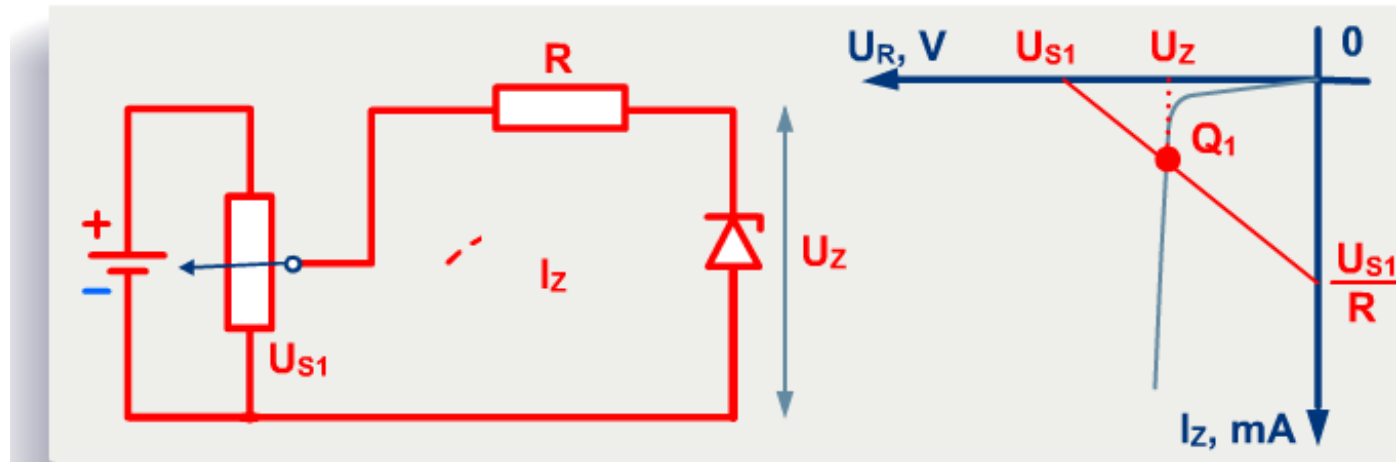

The load line can be plotted with its intercepts on the horizontal and vertical axes.

The interception point of a load line with the zener diode VA characteristic gives **operational point** of  $Q_1$ .


# Load Line Shifting

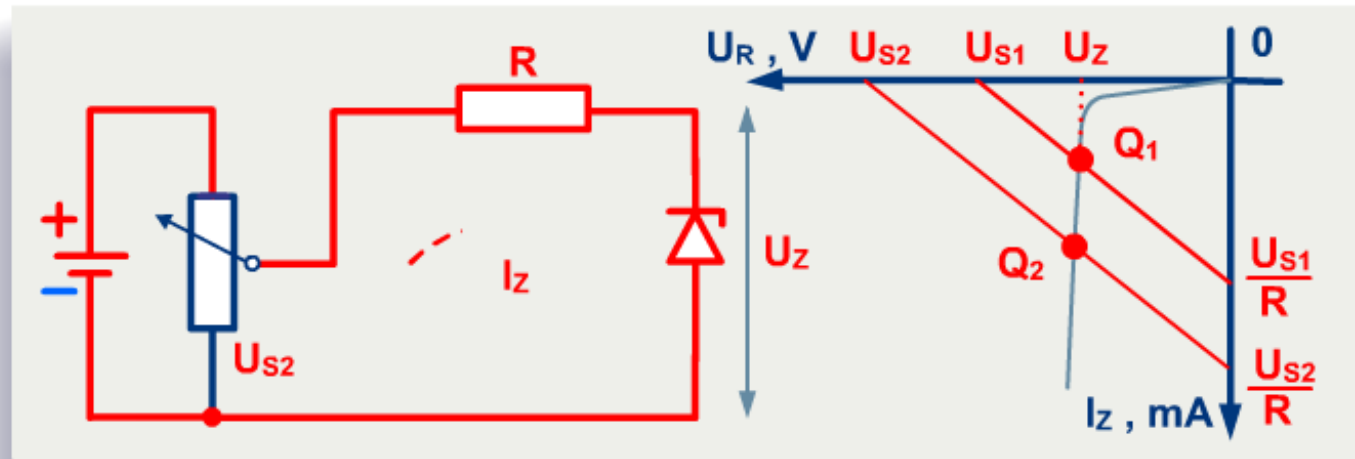

If the source voltage changes the zener current will also change. With  $R$  fixed the load line slope is unchanged but the  $U$  intercept shifts.

This is the basic idea of **voltage regulation** - the output voltage remained almost constant even though the input voltage changed by a large amount.


# Parameters – Zener Static Resistance

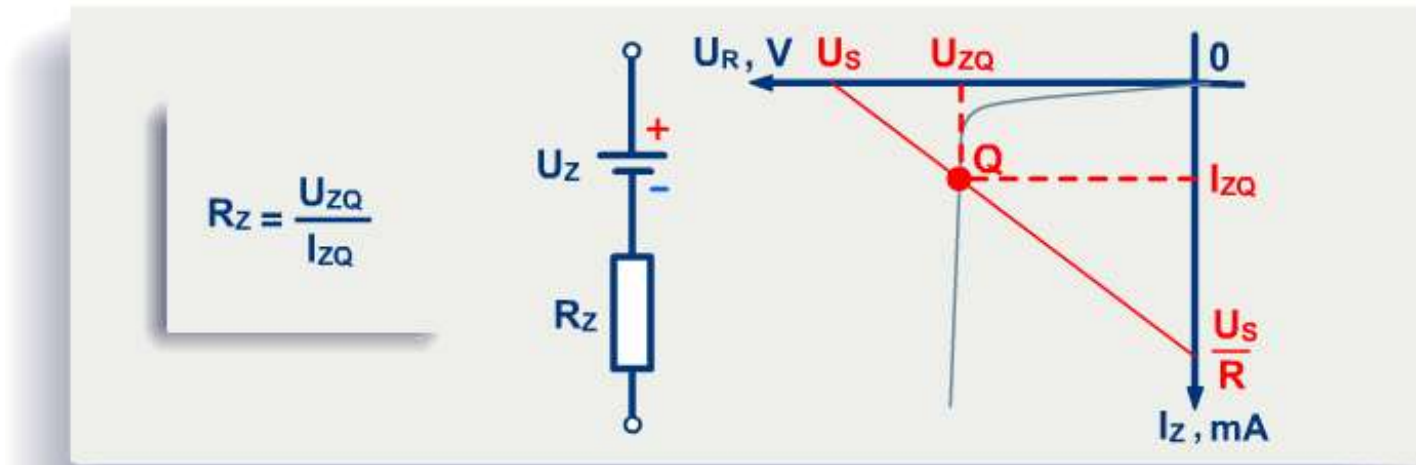

**Zener static** (or dc) **resistance**  $R_Z$  is the ratio of total zener diode voltage to total diode current measured at given operating point.


For more precise calculation a zener diode can be replaced by an ideal battery in series with a small zener resistance  $R_Z$ .

# Zener Dynamic Resistance

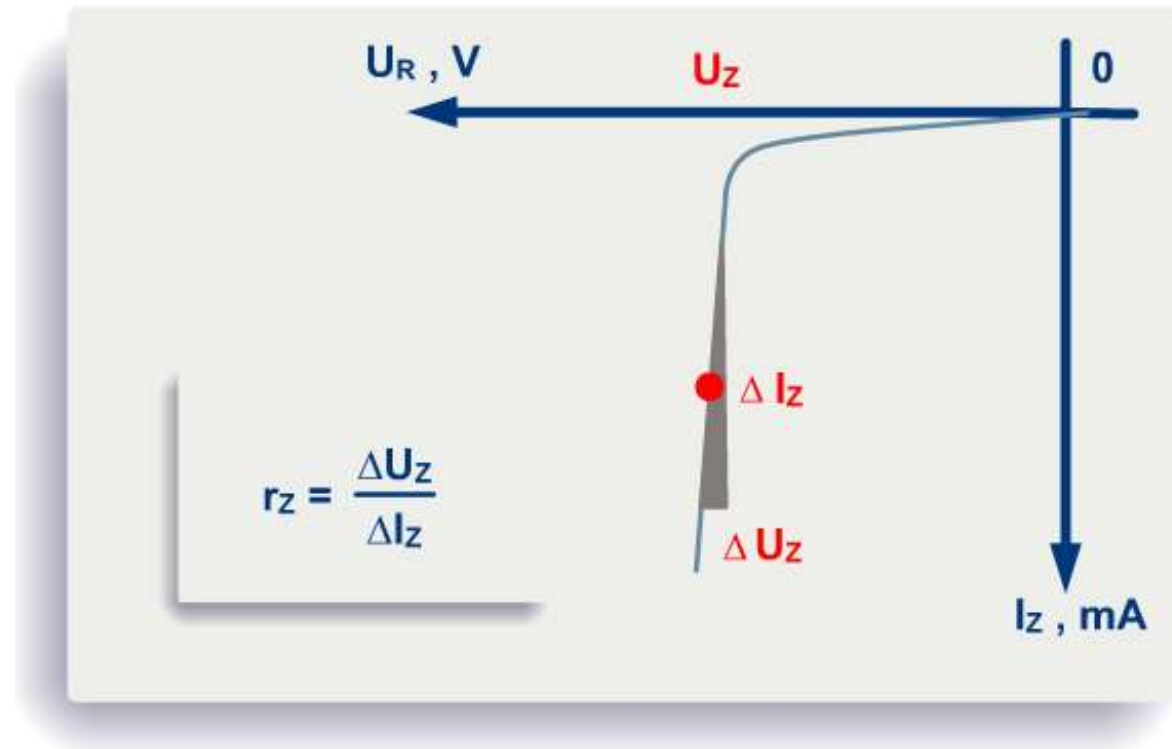


The **dynamic** (or ac) **zener resistance**  $R_Z$  is defined as voltage difference divided by current difference at given operating point. The less the dynamic resistance the better the zener diode as a voltage regulator.

# Zener Voltage

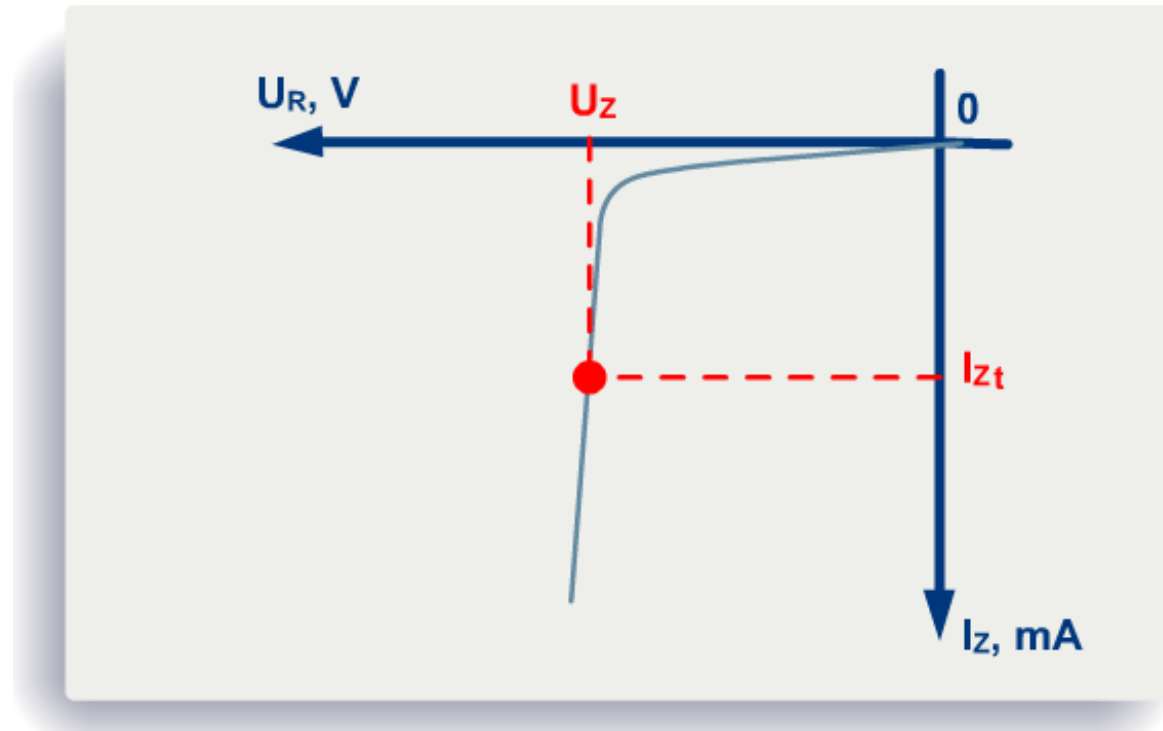


Zener diodes are available with the **zener breakdown voltage**  $U_Z$  in the range from several volts to several hundred volts. Data sheets usually specify the value  $U_Z$  at a particular current  $I_Z$ .

# Zener Voltage & Breakdown Effect

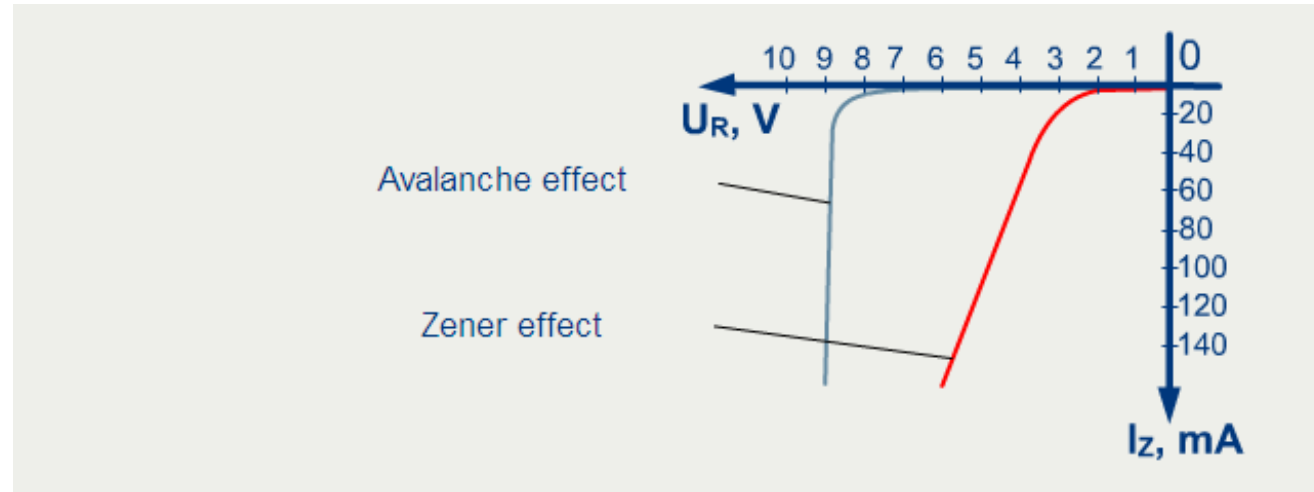

The **zener effect** occurs for **reverse voltages less than 5V**. **Avalanche effect** requires reverse **voltages above 6V**.


# Temperature Coefficient

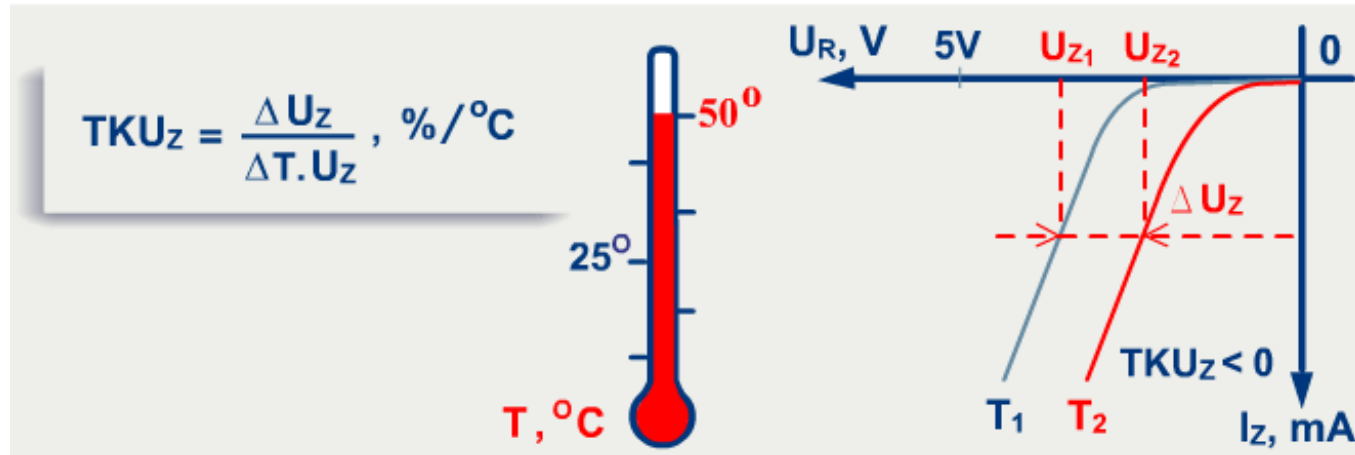

On data sheets, the effect of temperature is listed under the **temperature coefficient**, which is the percentage change per degree change.

For zener diode with **breakdown voltages of less than 5V**, the **temperature coefficient is negative**.

# Termo Compensation

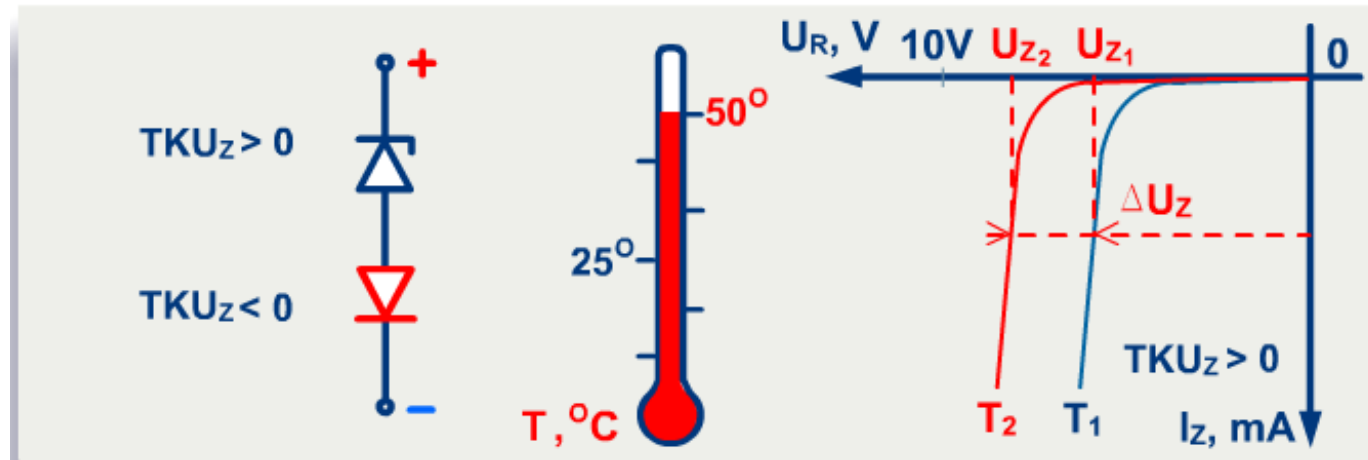


For zener diode with  $U_z > 6\text{V}$ , the **temperature coefficient is positive**.

Positive temperature coefficient can be compensated by connecting a zener diode in series with forward based *pn* junction diode. A forward biased ***pn* diode has negative temperature coefficient** and its forward voltage decreases  $-2\text{ mV}/^\circ\text{C}$ .




# Zener Diode Ratings

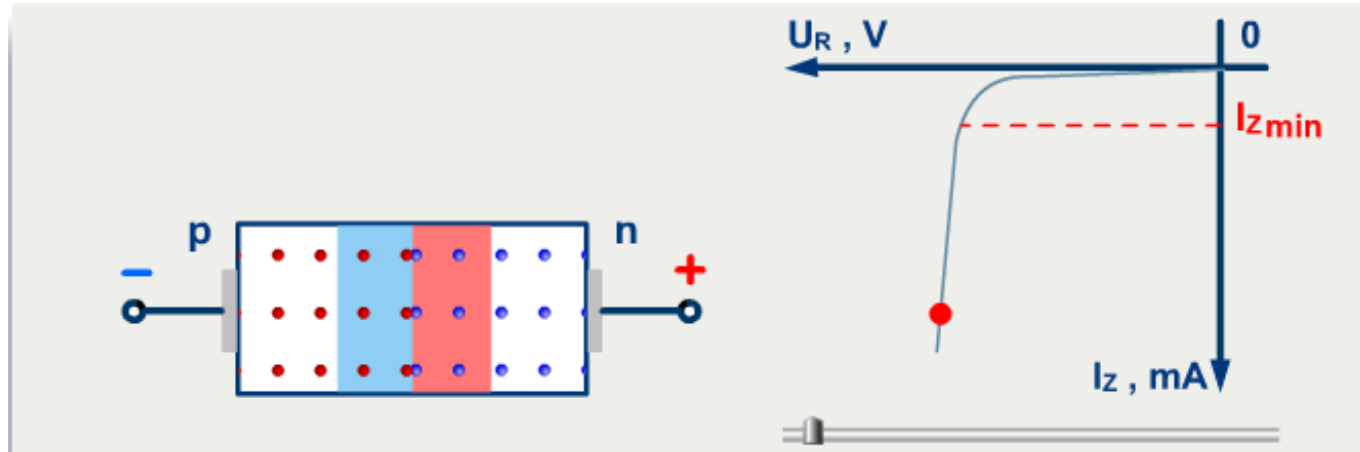


**Minimum zener current**  $I_{zmin}$  is the minimum reverse current where the breakdown becomes stable. If a zener diode has to remain in the breakdown region the current through it has to be more than  $I_{zmin}$ .

# Maximum Power

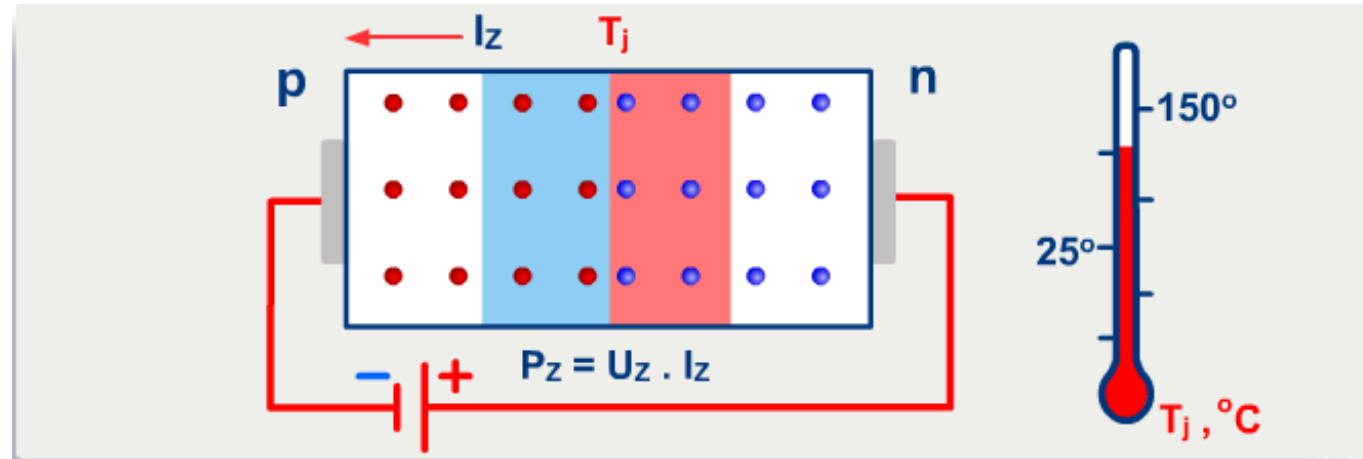


The power dissipation of a zener diode equals the product of its zener voltage and current  $P_z = U_z \cdot I_z$ . As long as  $P_z$  is less than the **maximum power rating**  $P_{z\max}$  the zener diode can operate in the breakdown region without being destroyed.

# Maximum Current

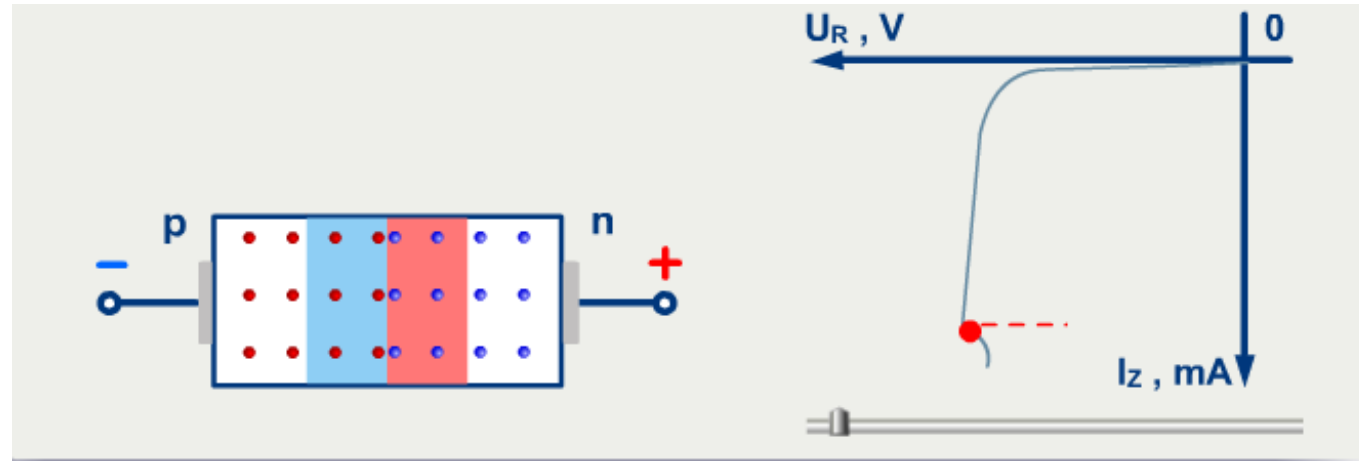


The maximum current of a zener diode  $I_{Zmax}$  is related to the power rating  $P_{Zmax}$  as follows:  $I_{Zmax} = P_{Zmax} / U_Z$ , where  $U_Z$  is the zener voltage. This parameter gives the max current a zener diode can handle without exceeding its power rating.

# Current-Limiting Resistor

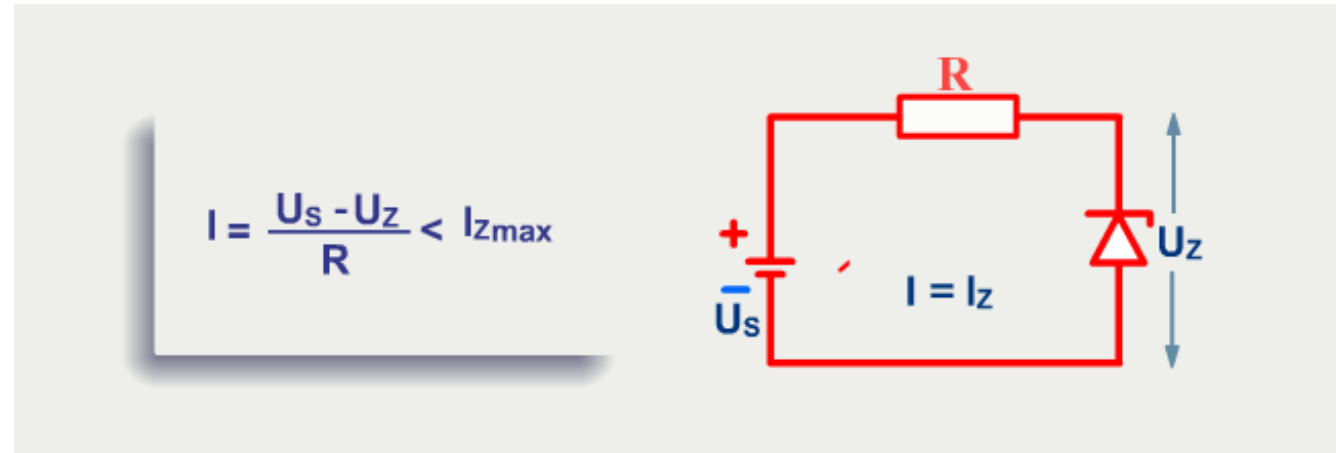

In the figure, the series resistor  $R$  is referred to as a **current-limiting resistor**. Its purpose is to keep the zener current less than its maximum current rating  $I_{zmax}$ . The zener diode will otherwise be destroyed like any device exposed to power overload.

# Loaded Voltage Regulator

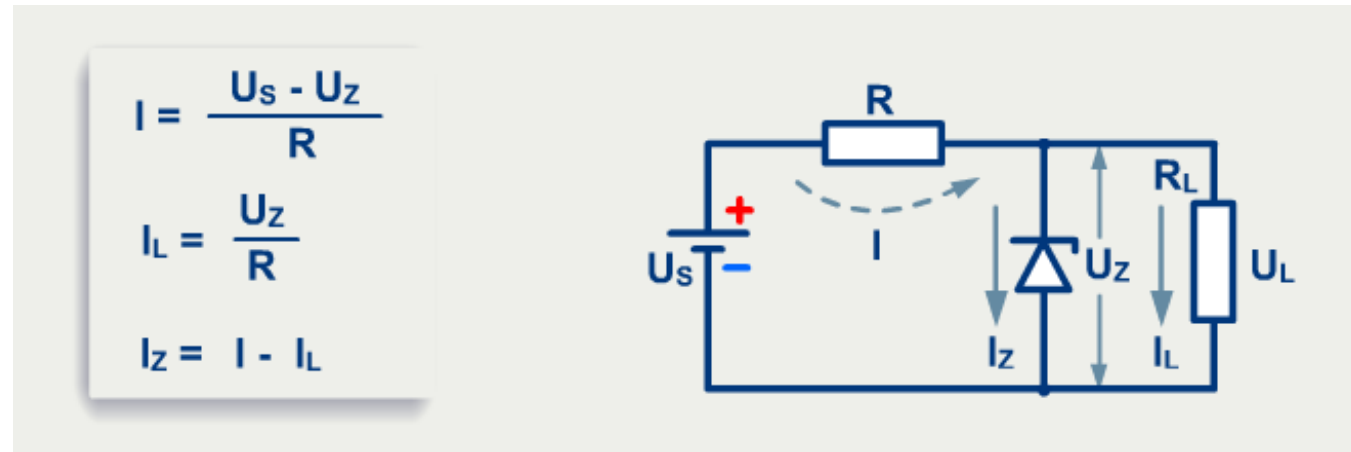


Currents in the circuit

Loaded voltage regulator

The zener diode **holds the load voltage constant despite large changes in source voltage or in load resistance.**

# Voltage Limiter

## Half-wave Zener diode clipping

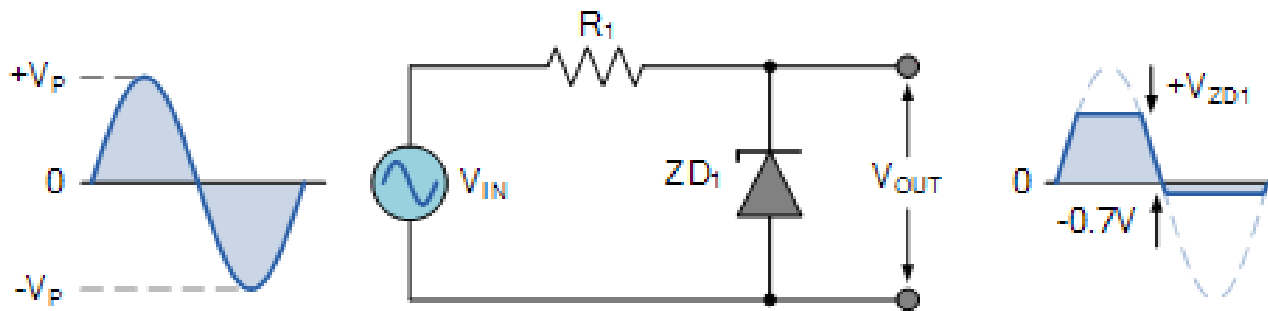


**Voltage limiter** removes signal voltages above or below a specified level. It is useful not only for signal shaping but also for protecting the circuits that receive the signal.

In this circuit during the positive half of the waveform the Zener diode is reverse biased so the waveform is clipped at the Zener voltage,  $V_{ZD1}$ . During the negative half cycle the Zener acts like a normal diode with its usual  $0.7V$  junction value.


# Voltage Limiter

## Full-wave Zener diode clipping

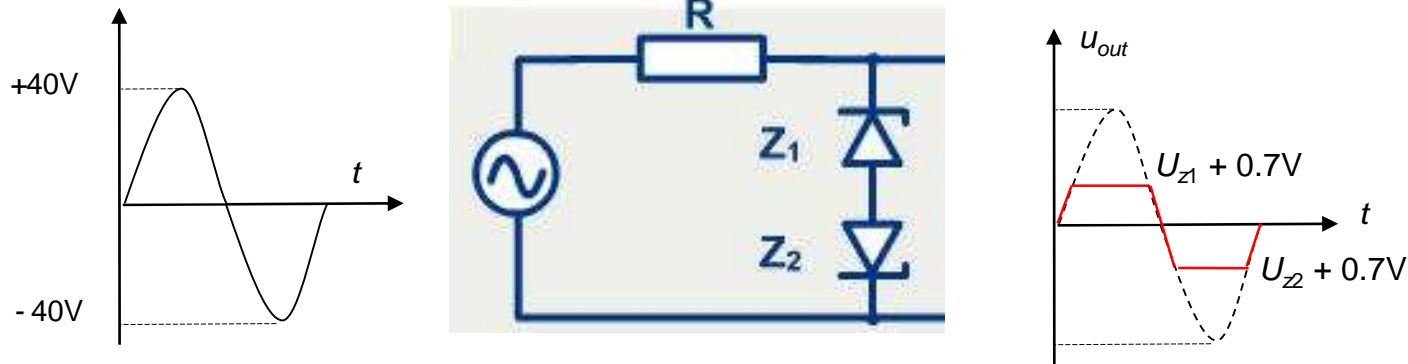

On the positive half cycle, the diode  $Z_1$  breaks down and the diode  $Z_2$  is forward biased. The output is then clipped. The clipping level equals the Zener voltage  $U_Z$  of Zener diode plus 0.7V of forward-biased diode.


# Examples

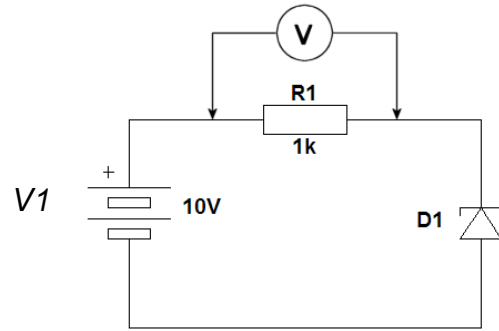

$$U_z = 8.2V$$


$V1 > U_z$  Diode is in the breakdown region with  $U_z = 8.2V$  over it

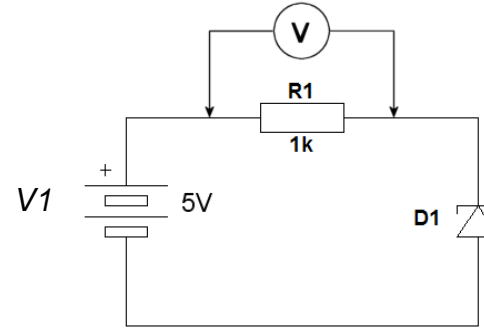$U_r = V1 - U_d = 10 - 8.2 = 1.8V$   
according Kirchhoff law



$V1 < U_z$  Diode is in the reverse connection,  $I = 0$

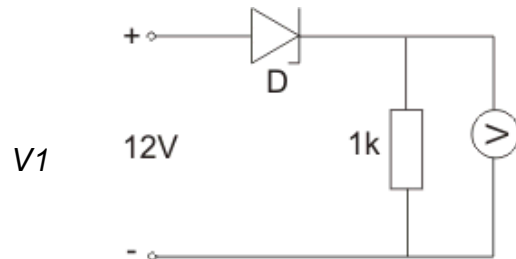
$U_r = I \cdot R = 0V$ , according Ohm's law  
 $U_d = V1 - U_r = V1 = 5V$ , according Kirchhoff law



$$U_z = 9V$$

$V1 > U_z$   
breakdown region

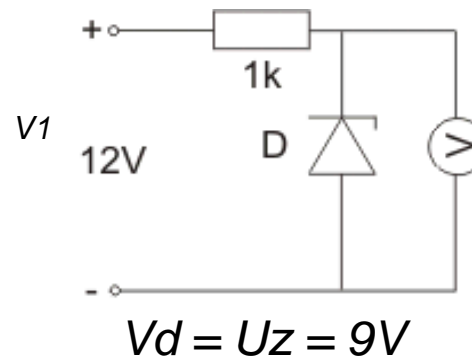$U_r = V1 - U_d = 12 - 9 = 3V$   
according Kirchhoff law



$$V_d = U_z = 9V$$